



Surname, Name:

Time: 1h. 40'

Question 1.1 (0.25 points)

Given the decimal integer numbers $A = 88$ and $B = -50$.


- Represent A and B in 2's complement with the minimum possible number of bits.
- Using 2's complement representations for the numbers, perform the operations $A-B$ and $A+B$. Point out if there is overflow in any of this operations and why.

Question 1.2 (0.25 points)

- Draw the 3-bit Gray's Code
- Draw the 3-bit Johnson's Code

Question 1.3 (0.25 points)


Draw the truth table of the following circuit:

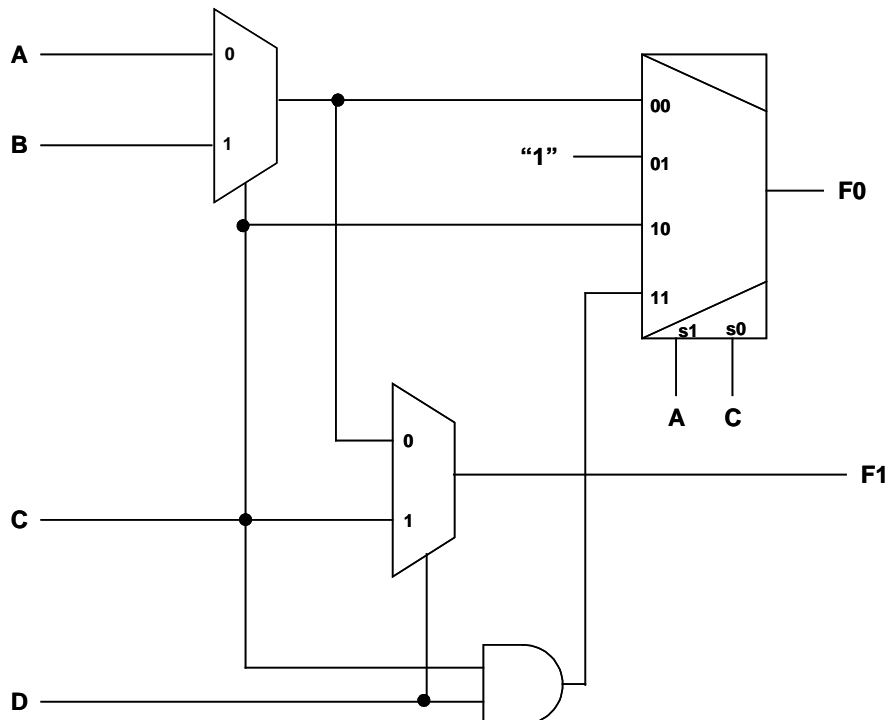



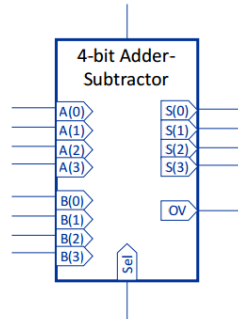Question 1.4 (0.25 points)


We want to design the following circuit (a 4-bit adder/subtractor).



Where A and B are the data inputs (4-bit), S is the data output (4-bit), Sel is the operation selection ('0' means addition and '1' means subtraction), and OV is an overflow indicator (it is active-high, and it is activated when there is overflow in the operation).

To design this circuit we have available the following components:

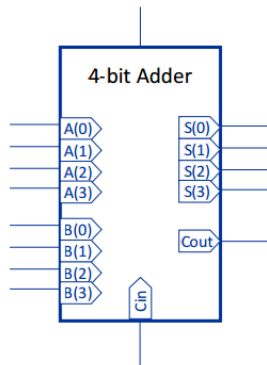- Logic gates
- A 4-bit adder like the one of the figure:



Where A and B are the data inputs (4-bit), S is the data output (4-bit), and Cin/Cout are the carry-in and carry-out of the 4-bit adder.

Design the circuit using these available components.

Problem (1 points)

Given the following logic function:


$$f(a,b,c,d) = \overline{a}cd + \overline{b}(a + c + \overline{d})$$

- Find the most simplified logic expression as a sum of products
- Find the most simplified logic expression as a product of sums
- Implement the logic function with only 2-input NOR gates.
- Implement f with a 4:16 decoder and additional logic gates.
- Implement f with a MUX4 (multiplexer with 4 data inputs) and additional logic gates.



Universidad Carlos III de Madrid
Digital Electronics. 1st midterm exam. March, 2014
Groups 65-69-79-95


* Question 1. a) $A = 88$

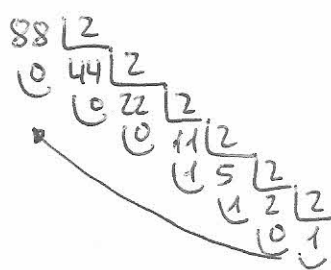

$$\Rightarrow 88_{10} = 1011000_2$$

01011000_{2C}
8 bits

$B = -50$

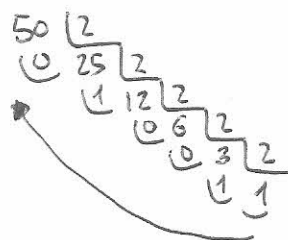

$$\Rightarrow 50_{10} = 110010_2 = 0110010_{2C}$$

\Rightarrow Therefore $-50_{10} = 1001110_{2C}$
7 bits

b) $A - B = 88 - (-50) = 88 + 50$

Adding zeros
because this is
a positive number

$$\begin{array}{r} 01011000 \text{ (+88)} \\ + 00110010 \text{ (+50)} \\ \hline 10001010 \text{ (+138)} \end{array}$$

There is overflow, because the sum of 2 positive numbers cannot be equal to a negative number. We can solve this using 9 bits for the operation


$A + B = 88 - 50$

Adding ones
because this is
a positive number


$$\begin{array}{r} 01011000 \text{ (+88)} \\ + 11001110 \text{ (-50)} \\ \hline 00100110 \text{ (+38)} \end{array}$$

There is no overflow, because the result sign is perfectly OK


* Question 2. a) 3-bit Gray's code

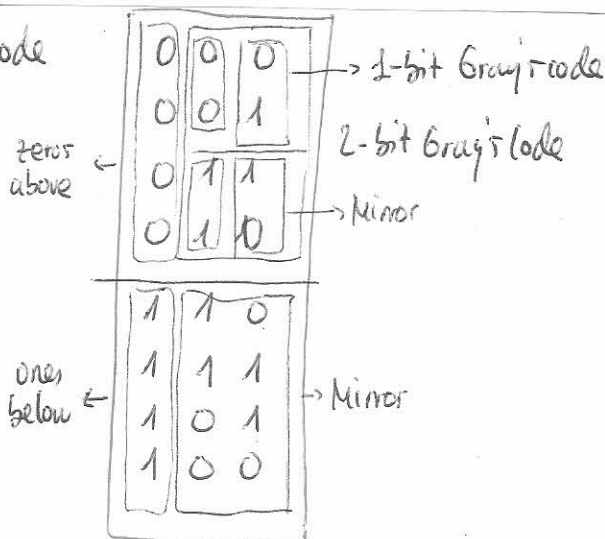

b) 3-bit Johnson's code

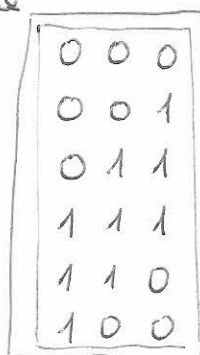

* Question 3

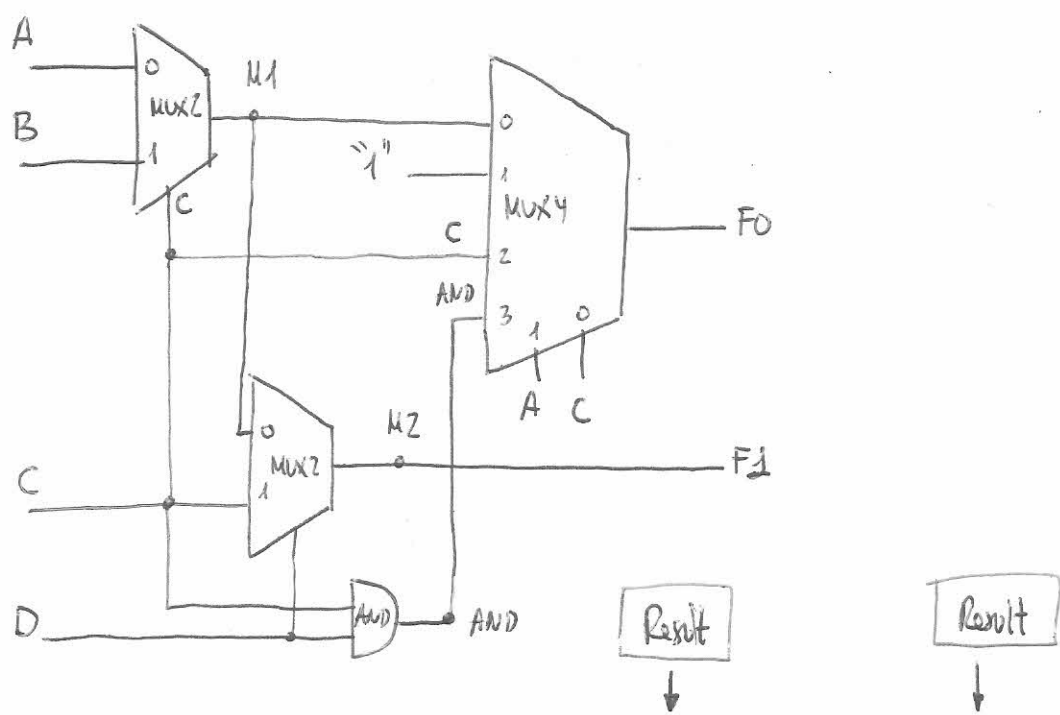

A	B	C	D	M1	M2 = F1	AND	F0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	1	1	1
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	1	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	1

$F0 = M1$ when $A=0, C=0$
 $F0 = 1$ when $A=0, C=1$
 $F0 = C$ when $A=1, C=0$
 $F0 = AND$ when $A=1, C=1$

$M1 = A$ when $C=0$
 $M1 = B$ when $C=1$


$AND = C * D$

$F1 = M1$ when $D=0$
 $F1 = C$ when $D=1$

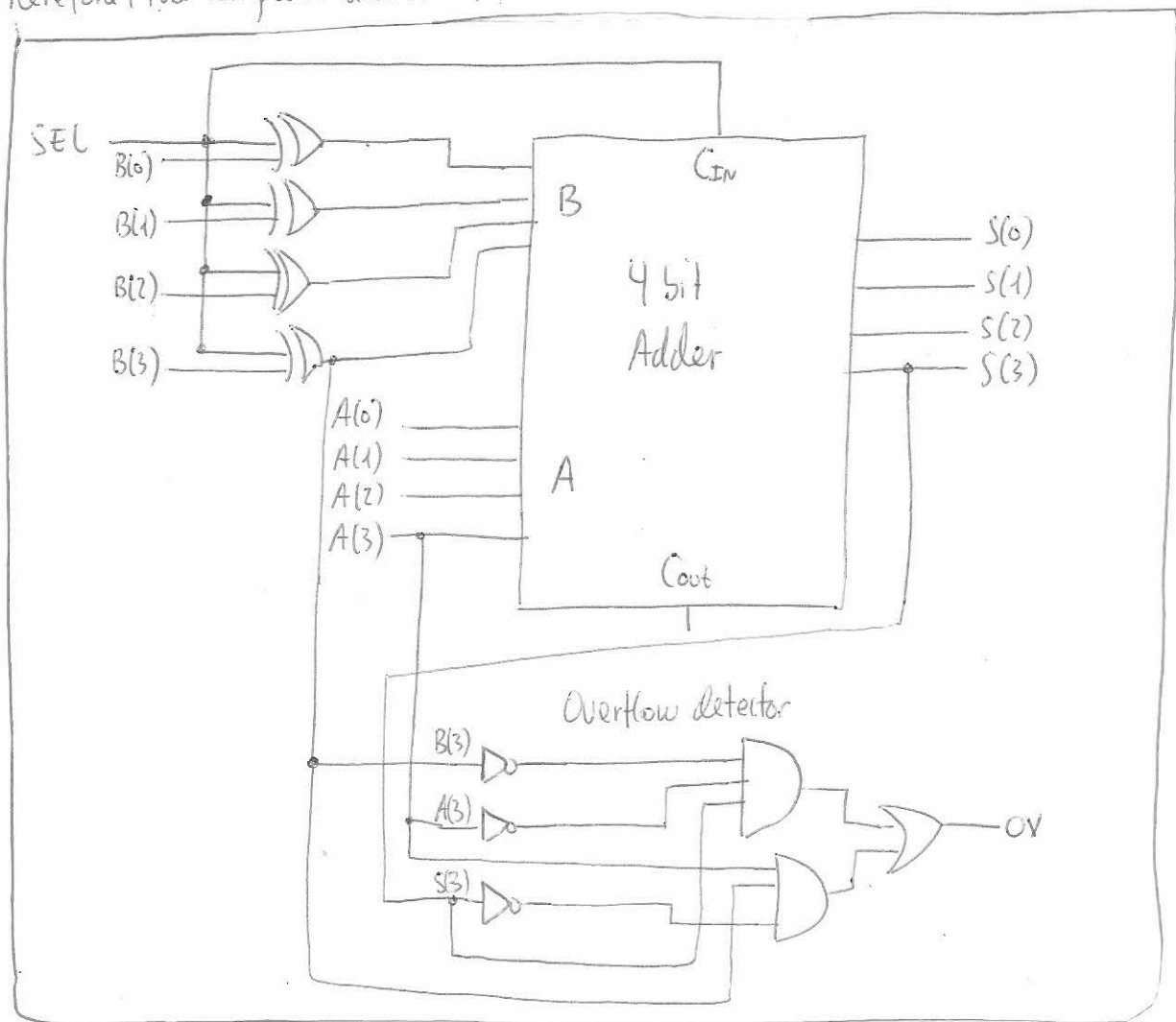* Question 4 : + You have to get the adder/subtractor circuit using the chip given. The trick is to add the necessary gates to this chip in order to get the desired circuit.

- + To subtract in 2-complement, first you have to get the 2-complement of a variable (for example, using the inversion of this variable and adding "1")
- + Now you have to add A and B using the select input to decide if you want to add A and B (addition) or to add A in 2-complement with B (subtraction)
- + You can obtain all of this using the SEL input and every bit of B with 4 XOR gates (connecting the 4 XOR outputs to the 4 B bits in the 4-bit adder) and besides connecting the SEL input to the C_{IN} input of the 4-bit adder, so that:
 - If $SEL=0$, B is not inverted, $C_{IN}=0$ and the operation is $A+B$, bit
 - If $SEL=1$, B is inverted, $C_{IN}=1$ and the operation is $A-B$
- + To obtain the OV circuit, it is necessary to do the truth table with the most significant bits of the Operands $A(3)$, $B(3)$ and $S(3)$, considering that there is overflow when the sign changes, that means $S(3)=1$ (negative number) when $A(3)=0$ and $B(3)=0$ (positive numbers), or $S(3)=0$ (positive number) when $A(3)=1$ and $B(3)=1$ (negative numbers):
$$OV = \overline{A(3)} \cdot \overline{B(3)} \cdot S(3) + A(3) \cdot B(3) \cdot \overline{S(3)}$$

+ Therefore, the complete circuit is the next one:



Problem: $f = f(a, b, c, d) = \bar{a} \cdot c \cdot d + \bar{b} (a + c + \bar{d}) = \bar{a} \cdot c \cdot d + a\bar{b} + \bar{b}c + \bar{b}\bar{d}$

• $\bar{a} \cdot c \cdot d = \bar{a} \cdot c \cdot d (b + \bar{b}) = \bar{a}bcd + \bar{a}\bar{b}cd$

• $a\bar{b} = a\bar{b}(c + \bar{c})(d + \bar{d}) = (a\bar{b}c + a\bar{b}\bar{c})(d + \bar{d}) = a\bar{b}cd + a\bar{b}\bar{c}d + a\bar{b}c\bar{d} + a\bar{b}\bar{c}\bar{d}$

• $\bar{b}c = \bar{b}c(a + \bar{a})(d + \bar{d}) = (a\bar{b}c + \bar{a}\bar{b}c)(d + \bar{d}) = a\bar{b}cd + a\bar{b}\bar{c}d + \bar{a}\bar{b}cd + \bar{a}\bar{b}\bar{c}d$

• $\bar{b}\bar{d} = \bar{b}\bar{d}(a + \bar{a})(c + \bar{c}) = (a\bar{b}\bar{d} + \bar{a}\bar{b}\bar{d})(c + \bar{c}) = a\bar{b}c\bar{d} + a\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}\bar{d}$

Therefore: $f = \bar{a}bcd + \bar{a}\bar{b}cd + a\bar{b}cd + a\bar{b}\bar{c}d + a\bar{b}c\bar{d} + a\bar{b}\bar{c}\bar{d} + a\bar{b}\bar{c}d + a\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd + \bar{a}\bar{b}\bar{c}d + a\bar{b}c\bar{d} + a\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}\bar{d}$

So:

a	b	c	d	f	position
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	1	2
0	0	1	1	1	3
0	1	0	0	0	4
0	1	0	1	0	5
0	1	1	0	0	6
0	1	1	1	1	7
1	0	0	0	1	8
1	0	0	1	1	9
1	0	1	0	1	10
1	0	1	1	1	11
1	1	0	0	0	12
1	1	0	1	0	13
1	1	1	0	0	14
1	1	1	1	0	15

and

ab \ cd	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

a) Sum of products $\rightarrow 1^{st}$ canonical form:

ab \ cd	00	01	11	10
00	1	1	1	
01		1		
11				
10	1	1	1	1

Annotations: $\bar{b}\bar{d}$ (circles at (00,0), (00,1), (10,0), (10,1)), $\bar{a} \cdot c \cdot d$ (circles at (01,1), (11,1), (10,1)), $a\bar{b}$ (circles at (10,0), (10,1), (10,1), (10,1))

$$f = \bar{b}\bar{d} + a\bar{b} + \bar{a}cd$$

b) Product of sums $\rightarrow 2^{nd}$ canonical form:


ab \ cd	00	01	11	10
00	1		1	1
01			1	
11				
10	1	1	1	1


Annotations: $a + c + \bar{d}$ (circles at (00,0), (00,1), (10,0), (10,1)), $\bar{b} + d$ (circles at (00,0), (00,1), (10,0), (10,1)), $\bar{a} + \bar{b}$ (circles at (00,0), (00,1), (10,0), (10,1))

$$f = (\bar{a} + \bar{b}) \cdot (\bar{b} + d) \cdot (a + c + \bar{d})$$

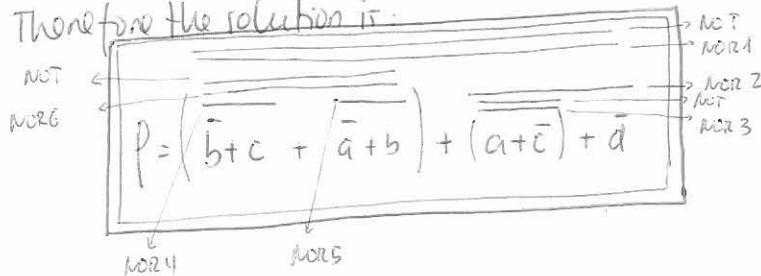
c) We use the first canonical form:

$$f = b\bar{c} + a\bar{b} + \bar{a}cd = \overline{\overline{b\bar{c} + a\bar{b} + \bar{a}cd}} = \overline{\overline{b\bar{c}} + \overline{a\bar{b}} + \overline{\bar{a}cd}} = \overline{\overline{b\bar{c}} + \overline{a\bar{b}} + \overline{\bar{a}} + \overline{c} + \overline{d}} = \overline{\overline{b\bar{c}} + \overline{a\bar{b}} + a + \bar{c} + \bar{d}}$$

- The not gate is implemented with a NOR gate with the same inputs \Rightarrow 
- The NOR with 3 inputs could be implemented as, for example, $(a + \bar{c}) + \bar{d}$ and the AND could be implemented as NOR + NOR
- Therefore the solution is:



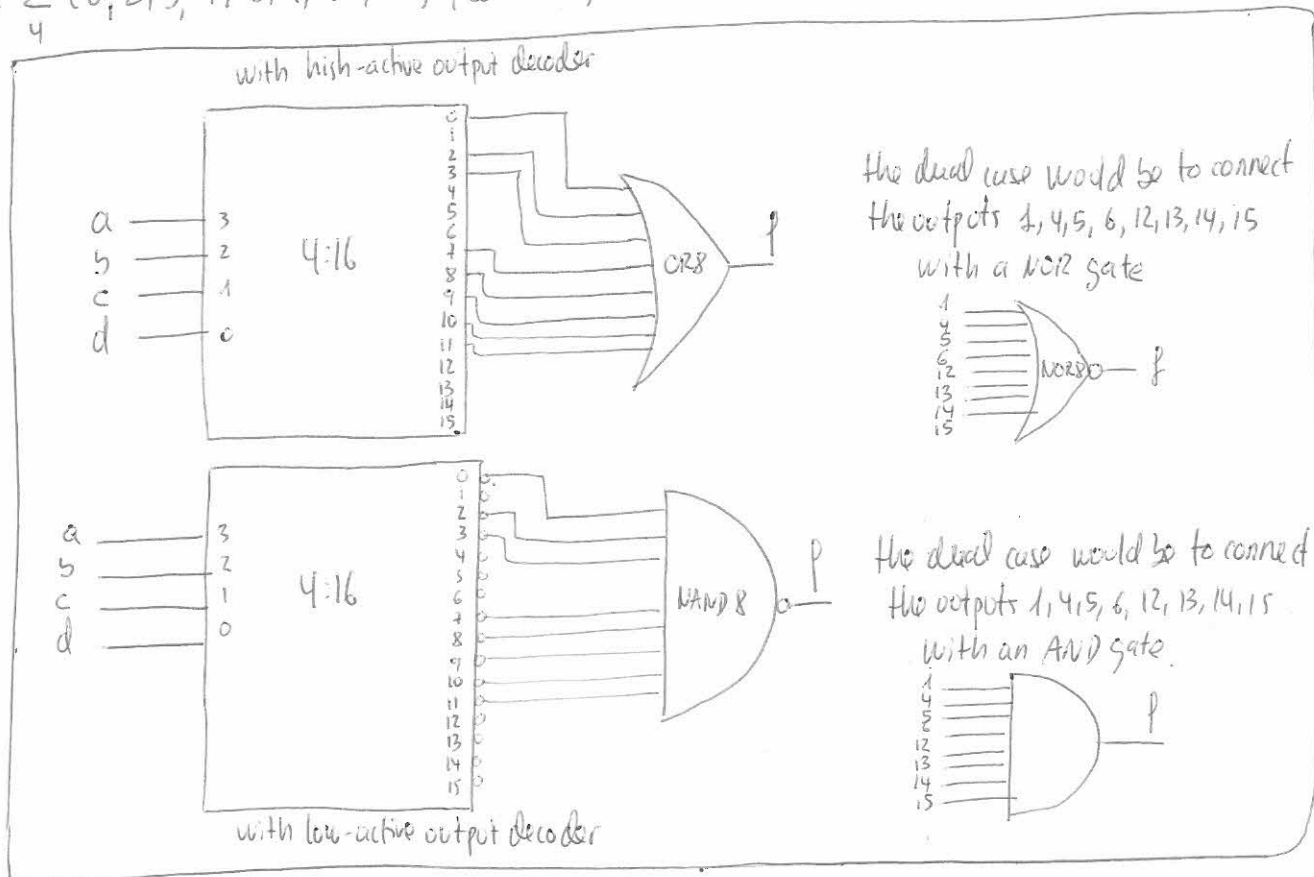d) $f = \sum_4 (0, 2, 3, 7, 8, 9, 10, 11)$, so looking at the truth table there are 4 solutions



e) Looking at the truth table:

