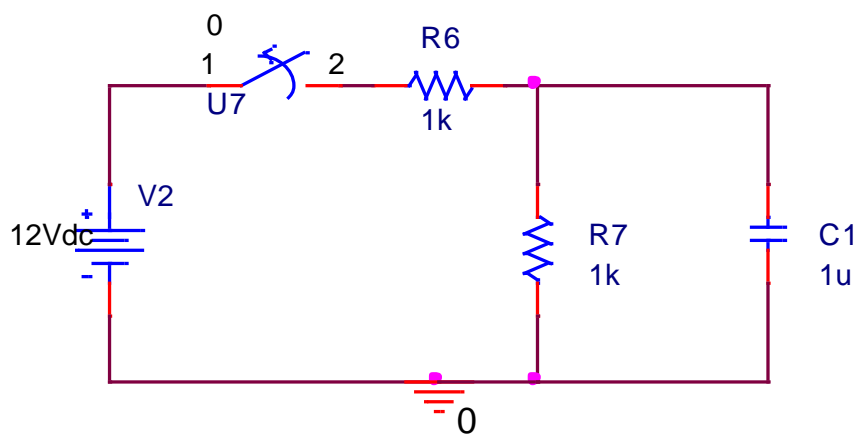


Problem

Given the circuit in next figure, where for $t < 0$ seconds, the switch U7 has been closed during a long time. At $t = 0$ seconds the switch is opened. (a) Find the time constant τ of the resulting circuit (3 points), (b) Find the equation of the voltage at the capacitor for $t \geq 0$ s (5 points), and (c) Compute the value and direction of the current at $t = \tau$ seconds (2 points). (All Resistances in kohms and capacitances in microFarads).



$$(a) \tau = 1k\Omega \cdot 1\mu F = 1ms$$

$$(b) v(t) = 6 \cdot e^{-\frac{t}{1ms}} \text{ V.} = 6 \cdot e^{-1000t} \text{ V.}$$

$$(c) i(t) = \frac{6}{1k\Omega} e^{-1000t} \text{ " } i(\tau) = \frac{6}{1k\Omega} \cdot \frac{1}{e} \text{ A} = 2,21 \text{ mA}$$

Counterclockwise