

### Question 1 (1 point not continuous evaluation, 0,5 points continuous evaluation):

Given a conductive loop that rotates within a magnetic field producing an electromotive force  $\varepsilon(t) = 4\pi \cdot \sin(2\pi t)$ , all magnitudes are expressed in international system units. This electromotive force is connected as the source of a circuit with impedance  $Z = 2\pi \angle 45^\circ \Omega$ .


- a) Obtain the expression of the magnetic flux in the loop as a function of time,

$$\phi = - \int 4\pi \cdot \sin(2\pi t) dt = 2 \cdot \cos(2\pi t) \text{ (S.I.)}$$

- b) Obtain the expression of the current flowing through the circuit as a function of time,


$$I(t) = 2 \cdot \sin(2\pi t - \pi/4) \text{ A.}$$

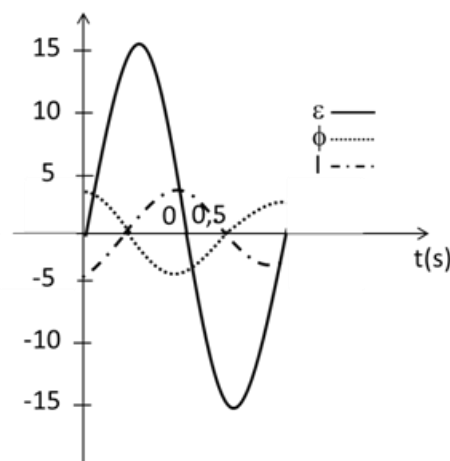- c) Draw a graph the magnetic flux, the current and the electromotive force in the interval  $t=0$  s y  $t=1$  s.


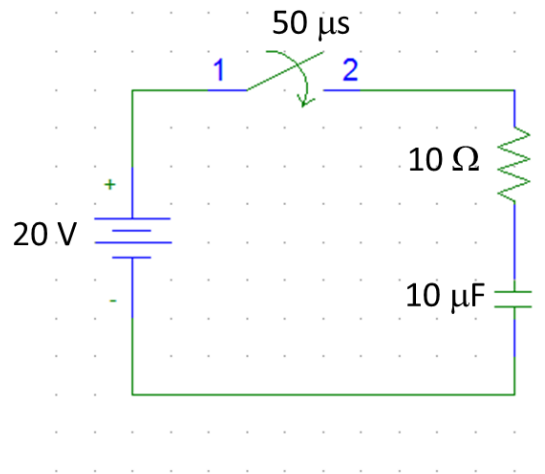
### Problem 1:( 2 point not continuous evaluation, 1,5 points continuous evaluation)

Given the circuit in next figure, where the capacitor is initially uncharged, and the switch is closed at  $t=50 \mu\text{s}$ .



- a) What is the maximum charge stored in the capacitor

$$Q_{\max} = CV = 10 \cdot 10^{-6} \cdot 20 = 0.2 \text{ mC} = 200 \mu\text{C}$$

- b) What is the value of the time constant of the circuit and what is its meaning?

$$\tau = RC = 10 \cdot 10^{-6} = 0.1 \text{ ms} = 100 \mu\text{s}$$

- c) What is the value of the charge stored in the capacitor at instants:  $t=0 \mu\text{s}$ ,  $t=75 \mu\text{s}$ ,  $t=150 \mu\text{s}$  y  $t=200 \mu\text{s}$ ?

$$Q(t) = 200 \mu\text{C} \left( 1 - e^{-\frac{t-50 \mu\text{s}}{100 \mu\text{s}}} \right)$$

$$Q(0 \mu\text{s}) = 0 \text{ C (ya que no ha empezado el proceso de carga)}$$

$$Q(75 \mu\text{s}) = 200 \mu\text{C} \left( 1 - e^{-\frac{(75-50) \mu\text{s}}{100 \mu\text{s}}} \right) = 44.24 \mu\text{C}$$

$$Q(150 \mu\text{s}) = 200 \mu\text{C} \left( 1 - e^{-\frac{(150-50) \mu\text{s}}{100 \mu\text{s}}} \right) = 126 \mu\text{C}$$

$$Q(200 \mu\text{s}) = 200 \mu\text{C} \left( 1 - e^{-\frac{(200-50) \mu\text{s}}{100 \mu\text{s}}} \right) = 155 \mu\text{C}$$

- d) Obtain the expression of the current flowing through the circuit as a function of time.

$$I(t) = \frac{dQ(t)}{dt} = \frac{200 \mu\text{C}}{100 \mu\text{s}} \left( e^{-\frac{t-50 \mu\text{s}}{100 \mu\text{s}}} \right) = 2 \text{ A} \cdot e^{-\frac{t-50 \mu\text{s}}{100 \mu\text{s}}}$$

## Problem2 2: (2 point not continuous evaluation, 1,5 points continuous evaluation)

Given the circuit in next figure, where  $V_L = 16 + 0j$  V.


- (a) Calculate the current I.

$$I = \frac{V_L}{Z_L} = \frac{16 \angle 0^\circ \text{ V}}{8 \angle 90^\circ \Omega} = 2 \angle -90^\circ \text{ A}$$

- (b) Calculate the impedance Z.

$$Z = -8j \Omega$$

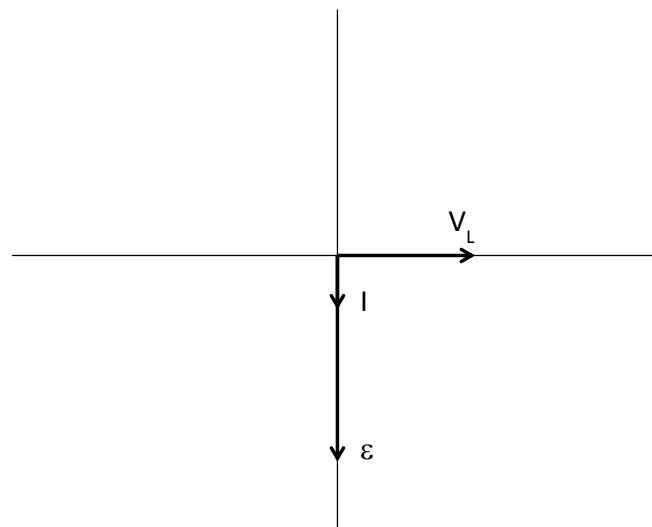
- (c) Draw the phasor diagram for voltage at the source, the current I and the voltage  $V_L$ .



- (d) Calculate the power factor and average power of the whole circuit and the power factor and average power at the inductance.

Power factor in inductance = 0, Av. Power Inductance = 0 W


Power factor in circuit = 1, Av Power in circuit = 24 W

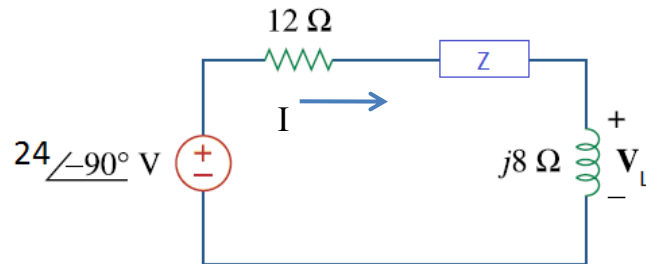

**Problem 3:( 2 point not continuous evaluation, 1,5 points continuous evaluation)**

Given the circuit in next figure. Calculate:

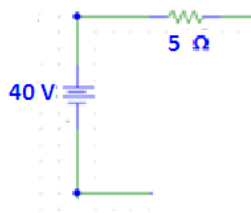1. Thevenin equivalent circuit across nodes A and B



2. The current through resistances R2 and R5.

$$I_{R2} = I_1 = 2 \text{ A}$$


$$I_{R5} = I_3 = 3 \text{ A}$$

3. Norton equivalent circuit through nodes A and B.

$$I_N = 8 \text{ A}$$

$$R_N = 5 \text{ ohms}$$

30/06/2015

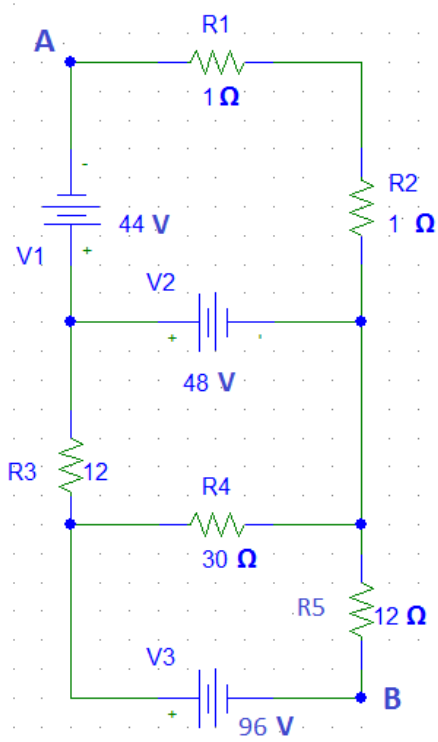

## Only for Not Continuous Evaluation Route

### Question 2: (1 point not continuous evaluation)

Given an AC circuit composed of a source and an impedance. The source is  $V(t) = 20 \sin 3t$ . The average power  $P$  is 200W and the reactive power  $Q$  is 40 W, as shown in next figure. Calculate:

- a) The value of the power factor. Explain the meaning of the value of this power factor.


$$\frac{P(react)}{P(act)} = \frac{40}{200} = 0.2 = \tan \phi$$

$$\tan \phi = 0.2 \quad \phi = 11.31^\circ$$

$$\cos \phi = 0.98$$

- b) The apparent power (S).

$$S = \sqrt{P^2 + Q^2} = 204 \text{ W}$$

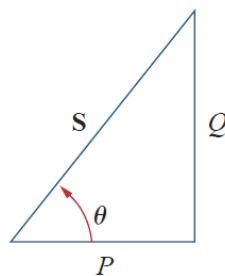

### Problem 4: (2 point not continuous evaluation)

Given a series RLC circuit with an AC voltage source. The current through the circuit is  $I(t) = (10 \text{ mA}) \cdot \cos(10t + \pi/4)$ . The inductor  $L$  of the circuit is a very long solenoid with radius  $R = 2 \text{ cm}$ , and  $n = 10$  turns/m. Inside  $L$  there is a coaxial circular coil with  $N = 10$  turns of  $r = 1 \text{ cm}$  radius, and  $10 \Omega$  resistance. Calculate:

- a) The magnetic flux in the inside coaxial coil due to the magnetic field produced by the solenoid L.

$$\Phi = N\pi r^2 \mu_0 n I_0 \cos(\omega t + \phi_1) = 10 \cdot \pi \cdot (0.01)^2 \cdot 4 \cdot \pi \cdot 10^{-7} \cdot 10 \cdot 10 \cdot 10^{-3} \cdot \cos(10t + \pi/4) =$$

$$= 3.95 \cdot 10^{-10} \cdot \cos(10t + \pi/4) \text{ Wb}$$

- b) The induced emf in the inside coaxial coil.

$$\varepsilon = -d\Phi/dt = N\pi r^2 \mu_0 n I_0 \omega \sin(\omega t + \phi_1) = 10 \cdot \pi \cdot (0.01)^2 \cdot 4 \cdot \pi \cdot 10^{-7} \cdot 10 \cdot 10 \cdot 10^{-3} \cdot 10 \cdot \sin(10t + \pi/4) =$$

$$= 3.95 \cdot 10^{-9} \cdot \sin(10t + \pi/4) \text{ V}$$

- c) The magnitude and direction of the current in the inside coaxial coil.

$$I = \varepsilon/R = N\pi r^2 \mu_0 n I_0 \omega \sin(\omega t + \phi_1)/R = 10 \cdot \pi \cdot (0.01)^2 \cdot 4 \cdot \pi \cdot 10^{-7} \cdot 10 \cdot 10 \cdot 10^{-3} \cdot 10 \cdot \sin(10t + \pi/4)/10 = 3.95 \cdot 10^{-10} \cdot \sin(10t + \pi/4) \text{ A}$$

- d) The capacitance C given that the resistance R is 5  $\Omega$  and the solenoid L has an inductance of 1 H, taking the reference phase of voltage the voltage source.

$$\phi_Z = \arctg((\omega L - 1/\omega C)/R) = \arctg((10 \cdot 1 - 1/10 \cdot C)/5) = -45^\circ$$

$$(10 \cdot 1 - 1/10 \cdot C)/5 = -1 \rightarrow 10 - 1/10C = -5 \rightarrow 15 = 1/10C \rightarrow C = 1/150 \text{ F} = 6.67 \cdot 10^{-3} \text{ F}$$

- e) The voltage of the source as a function of time.

$$Z = 5 + j(10 - 15) = 5 - 5j \Omega$$

$$\varepsilon = I \cdot Z = (10 \cdot 10^{-3} \text{ A}) \angle 45^\circ \cdot ((50)^{1/2} \Omega) \angle -45^\circ = 0.0707 \angle 0^\circ \text{ V}$$

$$\varepsilon(t) = 0.0707 \cos(10t) \text{ V}$$

$$\text{Data: } \mu_0 = 4\pi \cdot 10^{-7} \text{ Tm}$$