

NAME AND SURNAME:

GROUP:

Problem 1 (2,5 puntos)

A 4-bit data package (**D**) is transmitted on a telecommunication channel. We want to design a combinational circuit that implements the following functionality:

- Output **Parity (1 bit)**. Compute the odd-parity bit of the transmitted data.
 - Output **Difference (multiple bits)**. Compute using 2s-complement the difference between the number of 0's and 1's (0's -1's) of the 4-bit transmitted.
- a) Describe using VHDL the entity of the circuit. Explain the election of the data type and how this election will affect the architecture.

```
1 ENTITY Problem_1 IS
2 PORT(
3   D: IN STD_LOGIC_VECTOR (3 downto 0);      --4 bit input (must be converted to signed/unsigned to use arithmetic operations
4   Parity: OUT STD_LOGIC;                    -- 1-bit the result of the XOR/XNOR of the different bits of D
5   Difference: OUT STD_LOGIC_VECTOR (3 downto 0) -- 4 bit output necessary to represent numbers from +4 to -4
6 );
7 END Problem 1;
```

- b) Truth Table of the system.

D3	D2	D1	D0	Parity	Difference3	Difference2	Difference1	Difference0	DEC
0	0	0	0	1	0	1	0	0	+4
0	0	0	1	0	0	0	1	0	+2
0	0	1	0	0	0	0	1	0	+2
0	0	1	1	1	0	0	0	0	0
0	1	0	0	0	0	0	1	0	+2
0	1	0	1	1	0	0	0	0	0
0	1	1	0	1	0	0	0	0	0
0	1	1	1	0	1	1	1	0	-2
1	0	0	0	0	0	0	1	0	+2
1	0	0	1	1	0	0	0	0	0
1	0	1	0	1	0	0	0	0	0
1	0	1	1	0	1	1	1	0	-2
1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	1	1	0	-2
1	1	1	0	0	1	1	1	0	-2
1	1	1	1	1	1	1	0	0	-4

NAME AND SURNAME:

GROUP:

Problem 2 (4 puntos)

a) Obtain the equivalent schematic for the following VHDL code.

```



1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY exam IS
5      PORT
6      (
7          A : IN  STD_LOGIC_VECTOR (1 downto 0);
8          B : IN  STD_LOGIC_VECTOR (1 downto 0);
9          Y : OUT STD_LOGIC;
10         Z : OUT STD_LOGIC
11     );
12 END exam;
13
14 ARCHITECTURE bdf_type OF exam IS
15
16     SIGNAL AUX1,AUX3: STD_LOGIC;
17     SIGNAL S,AUX2:STD_LOGIC_VECTOR (1 downto 0);
18
19 BEGIN
20
21     S<=A(1) & B(1) ;
22     AUX1<=A(0) AND B(0) ;
23
24     PROCESS (S,AUX1,AUX2)
25     BEGIN
26     CASE S IS
27     WHEN "00" => z <= AUX1;
28     WHEN "01" => z <= AUX2(0) ;
29     WHEN "10" => z <= AUX2(1) ;
30     WHEN OTHERS => z <= S(0) ;
31     END CASE;
32     END PROCESS;
33
34
35
36     AUX2 <= "11" WHEN B(1) = '1' ELSE
37     "10" WHEN B(0) = '1' ELSE
38     "01" WHEN A(1) = '1' ELSE
39     "00";
40     AUX3 <= '1' WHEN A = "00" AND B = "00" ELSE
41     '0';
42
43     Y<=AUX3;
44
45 END bdf_type;

```

NAME AND SURNAME:

GROUP:

  b) Draw the values of Z and Y in the following chronogram.




NAME AND SURNAME:

GROUP:

 Problema 3(2 puntos)

Write a VHDL process that implements the functionality of the following schematic:



```

PROCESS (S,A,B)
BEGIN
CASE S IS
WHEN "00" => f <= A AND B;
WHEN "01" => f <= '0';
WHEN "10" => f <= A AND B;
WHEN OTHERS => f <= NOT B;
END CASE;
END PROCESS;

```

NAME AND SURNAME:

GROUP:

Problema 4(1,5 puntos)

- 1) The binary representation of the decimal number 37,3125
 a) **100101,0101**
 b) 101001,0101
 c) 100101,0110
 d) 101001,0110
- 2) Given the following numbers represented in CA2, A= 11000011 y B=01101100 determine their decimal value.
 A= **- 61** B= **+108**

Perform the following operations. There is overflow for the following operations? Why?

A+B = **00101111 (+47)** Overflow - YES **- NO**

A-B = **01010111 (Wrong)** Overflow **- YES** - NO

Why? **Using 8 bits, In two's complement we can represent number from:**

$-2^7 <-> 2^7 - 1 \rightarrow -128 - +127$

- 3) Fill the sensitivity list for the following process:

PROCESS (**A,B,C**)

BEGIN

X<= A OR B;

IF X='1' then

Y<='0';

ELSE

Y<='1';

END IF;

Z<= Y NAND C;

END PROCESS;