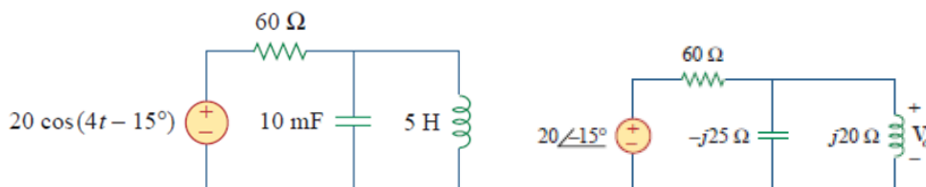


Problem 1 (5 points)

Given the AC circuit in the next figure. Calculate:


- The total equivalent impedance of the circuit.
- The maximum value of the current through the total equivalent impedance.
- The effective values for the voltage and current found in (b).
- The phasor representation for the current found in (b) and the voltage (Max Values).
- The power factor and average power for the total circuit.
- The maximum current through the 5H inductor branch.



(a) $Z_{eq} = (60 + 100j) \Omega = 116.62 \angle 59.04^\circ \Omega$

(b) $I_m = 0.17 \angle -74.04^\circ \text{ A}$

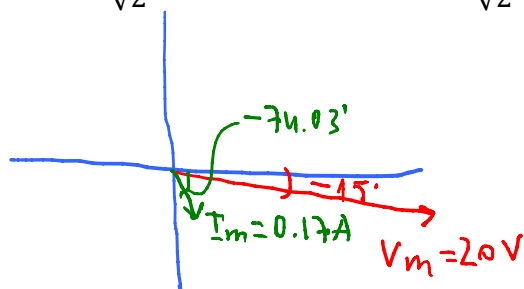(c) $V_{eff} = \frac{20}{\sqrt{2}} = 14.14 \text{ V}$, $I_{eff} = \frac{0.17}{\sqrt{2}} = 0.12 \text{ A}$



(d)


(e) $PF_{TOT} = \cos(-15^\circ - (-74.04^\circ)) = 0.51$, $P_{TOT_{av}} = V_{eff} \cdot I_{eff} \cdot PF_{TOT} = 0.87 \text{ W}$

(f) $V_{5H} = \frac{100j}{60 + 100j} 20 \angle -15^\circ = 17.20 \angle 15.96^\circ \text{ V}$,

$I_{5H} = V_{5H} / 20j = (17.20 \angle 15.96^\circ) / 20 \angle 90^\circ = 0.86 \angle -74.04^\circ \text{ A}$

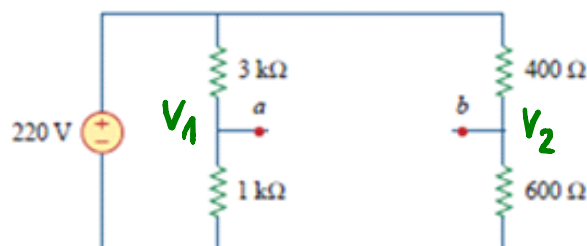Problem 2 (5 points)

Given the following DC circuit. Find across nodes a and b: (a) the Thevenin equivalent, (b) the Norton equivalent. Note: Do not use Source Transformation.



$$R_{Th} = 3000 \parallel 1000 + 400 \parallel 600$$


$$= \frac{3000 \times 1000}{3000 + 1000} + \frac{400 \times 600}{400 + 600} = 750 + 240 = 990 \Omega$$

(a)


$$v_1 = \frac{1000}{1000 + 3000}(220) = 55 \text{ V}, \quad v_2 = \frac{600}{600 + 400}(220) = 132 \text{ V}$$

Applying KVL around loop ab gives
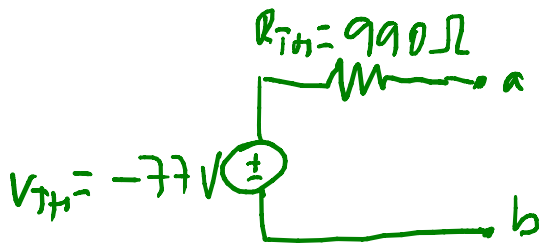
$$-v_1 + V_{Th} + v_2 = 0 \quad \text{or} \quad V_{Th} = v_1 - v_2 = 55 - 132 = -77 \text{ V}$$



(b) $R_N = 990 \, \Omega$

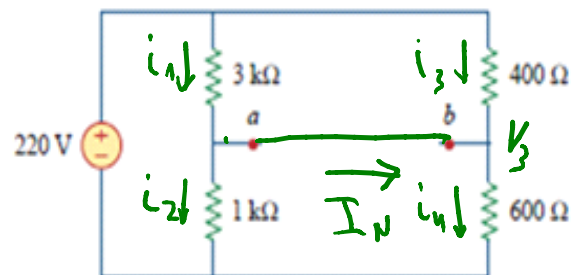

$$V_3 = 220 \cdot \frac{(1 \text{ k}\Omega \parallel 600 \, \Omega)}{(1 \text{ k}\Omega \parallel 600 \, \Omega) + (3 \text{ k}\Omega \parallel 400 \, \Omega)} = 220 \cdot \frac{375}{375 + 352.94} = 113.33 \text{ V}$$

$$I_1 = i_2 + I_N, \quad I_N = i_1 - i_2 = \frac{220 - 113.3}{3 \text{ k}\Omega} - \frac{113.3}{1 \text{ k}\Omega} = -0.08 \text{ A}$$

