

SURNAME, NAME:

GROUP:

Problem 1.1 (4 points; 30 minutes)

A control circuit has an enable input (E), 3 sensors (S) and three lights (G, Y, R). The circuit specifications are as follows:

- If the enable signal E is not active, all lights shall be off.
- If the enable signal E is active, then
 - o If all sensors are inactive, the green light (G) shall be on
 - o If at least one sensor is active, but not all of them, the yellow light (Y) shall be on.
 - o If all sensors are active, the red light (R) shall be on.

All signals are active high.

- a) Write the truth table of the circuit. Write the first canonical form (brief) of functions G, Y and R (1 p.).
- b) Implement the functions G, Y and R using a 3-input decoder with enable and the additional gates that may be needed (1.5 p.).
- c) Write a single VHDL process that implements the circuit as a pure combinational design, assuming the following declarations (1.5 p.):

SIGNAL S: STD_LOGIC_VECTOR(0 TO 2);

SIGNAL E: STD_LOGIC;

SIGNAL G, Y, R: STD_LOGIC;

SURNAME, NAME:

GROUP:

Problem 1.2 (3 points; 30 minutes)

Given the following VHDL code:

```
ARCHITECTURE final OF exam IS
-- Signal declaration

BEGIN

s<=a&b;

PROCESS (
)
BEGIN
CASE s IS
    WHEN "00" =>    e <= '0';
    WHEN "01" =>    e <= d nand a;
    WHEN "10" =>    e <= c xnor d;
    WHEN OTHERS =>  e <= '1';
END CASE;
END PROCESS;

PROCESS (
)
BEGIN
    f(0)<=a OR b;
    f(1)<=e;
END PROCESS;

WITH f SELECT
    z <= "0001" WHEN "00",
        "0010" WHEN "01",
        "0100" WHEN "10",
        "1000" WHEN OTHERS;

    x <= z(1 downto 0) AND z(3 downto 2);

END final;
```

a) Describe the entity of this circuit

- b) Declare the necessary signals (in the code)
- c) Fill the sensitivity lists (in the code)
- d) Draw the schematic. Do not forget to specify the components (e.g. mux, dec, enc, add, etc) and the lines that correspond to each component (in the code).

SURNAME, NAME:

GROUPp:

Problem 1.3 (3 points; 20 minutes)

- a) Complete the following table with the representation of numbers considering the different systems, using 8 bits. (0.2 p. each value, up to max. 1.5 points):

	A	B
Decimal		
Binario Natural		
Hexadecimal		4E
BCD		
OCTAL	44	

- a) Using **A** and **B** from part a), carry out the following operations in 2's complement (8 bits). Indicate if there is overflow, justifying it. If there is overflow, also indicate the correct solution.

A-B (0.75 points)

-A-B (0.75 points)