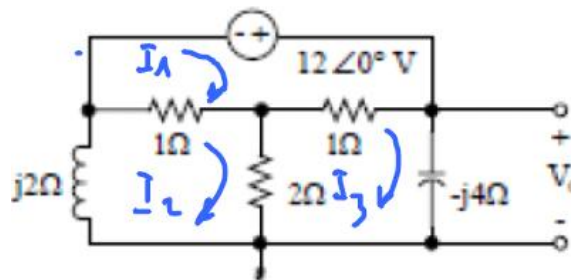


1. $\omega = 1 \text{ rad/s}$. (a) Use mesh analysis to find I_0 and V_0 in the network in next figure. (b) Find the average power and the power factor in the branch corresponding to I_0 .



$$I_3 = I_0$$

$$\textcircled{a} \quad \begin{aligned} 2I_1 - I_2 - I_3 &= 12 \angle 0^\circ \\ -I_1 + (3 + 2j)I_2 - 2I_3 &= 0 \\ -I_1 - 2I_2 + (3 - j4)I_3 &= 0 \end{aligned} \quad \begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 + 2j & -2 \\ -1 & -2 & 3 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$I_1 = 9.03 + 1.15j$$

$$I_2 = 4.04 - 0.67j$$



$$I_3 = 2.02 + 2.76j = I_0 \quad V_0 = (2 + 2.76j)(-j4) = 11.04 - 8.08j$$

$$I_0 = 3.42 \angle 53.8^\circ \quad V_0 = 13.68 \angle -36.2^\circ$$

$$\textcircled{b} \quad P_{av} = \frac{1}{2} I_0 \cdot V_0 \cdot \cos(\theta_{V_0} - \theta_{I_0}) = \frac{1}{2} 3.42 \cdot 13.68 \cos(90^\circ) = 0 \text{ W}$$

$$\text{Power factor} = \cos(90^\circ) = 0 \text{ Watt}$$

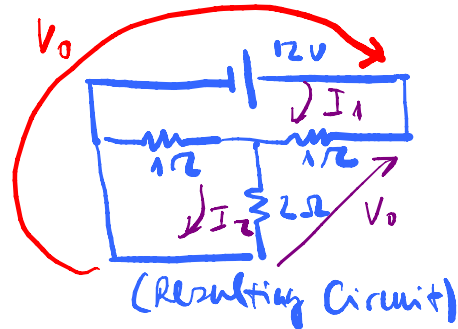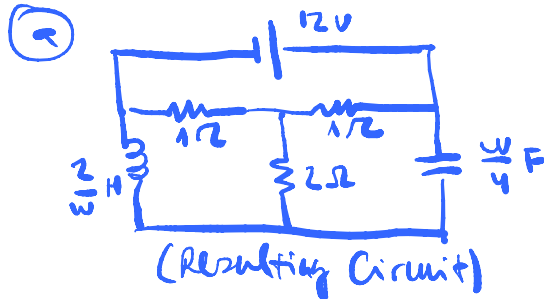2. Replace the AC source in the previous figure with a DC source of 12 V. (same polarity) (a) Draw the resulting circuit and the equivalent circuit for DC steady state analysis. (b) Use mesh analysis to find V_0 . (steady state). (c) Find the power dissipated in the 2 ohm resistance.



$$V_0 = I_1 \cdot 1\Omega + I_2 \cdot 2\Omega$$

OR $V_0 = 12\text{ V (also)}$

②

$$\begin{aligned} 2I_1 - I_2 &= 12 \\ -I_1 + 3I_2 &= 0 \end{aligned}$$

$$\begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.59 & 0.20 \\ 0.20 & 0.40 \end{bmatrix} \begin{bmatrix} 12 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.59 \times 12 \\ 0.20 \times 12 \end{bmatrix} = \begin{bmatrix} 7.2 \\ 2.4 \end{bmatrix}$$

$$I_1 = 7.2\text{ A}, I_2 = 2.4\text{ A}$$

$$V_0 = 7.2\text{ A} \cdot 1\Omega + 2.4\text{ A} \cdot 2\Omega = 12\text{ V}$$

③ $P = I_2^2 \cdot 2\Omega = 11.52\text{ W}$