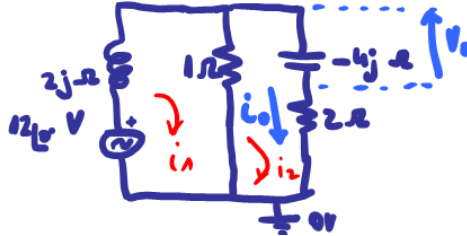


1. (5 points) In the following circuit. (a) Use mesh analysis to find  $I_0$  and  $V_0$  in the network in next figure ( $\omega = 1$  rad/s). (b) Find the average power and the power factor in the branch corresponding to  $I_0$ . ( $\omega = 1$  rad/s), and (c) Find the magnitude and phase of  $V_0$  as a function of  $\omega$ .



$$(a) \begin{cases} i_1(1+2j) - i_2 = 12 + 0j \\ -i_1 + i_2(3-4j) = 0 \end{cases} \rightarrow i_2 = \frac{\begin{vmatrix} 1+2j & 12 \\ -1 & 0 \end{vmatrix}}{\begin{vmatrix} 1+2j & -1 \\ -1 & 3-4j \end{vmatrix}} = \frac{12}{10+2j} A$$

$$i_2 = i_0 = \frac{25}{26} - \frac{5}{26}j A = 5\sqrt{\frac{1}{26}} \angle 2\pi - \arctan(1/5)$$

$$V_0 = \left(\frac{25}{26} - \frac{5}{26}j\right)(-4j) V = -\frac{10}{13} - \frac{50}{13}j = 10\sqrt{\frac{2}{13}} \angle \pi + \arctan(5) V$$

$$(b) P_{av} = \frac{1}{2} |i_0| \cdot |V_0| \cdot \text{Power factor} = \frac{1}{2} 5\sqrt{\frac{1}{26}} \cdot 10\sqrt{\frac{2}{13}} \cos(-\arctan(1/5) + \arctan(11/3))^\omega$$

$$V_0 = i_0 \cdot (2-4j) = \frac{15}{13} - \frac{55}{13}j = 5\sqrt{\frac{10}{13}} \angle 2\pi - \arctan(11/3) V$$

$$\text{Power factor} = \cos(\theta_{V_0} - \theta_{i_0}) = \cos(-\arctan(11/3) + \arctan(1/5))$$



$$-4j = -\frac{1}{C\omega}j, 2j = L\omega j \quad (\omega = 1) \rightarrow \begin{matrix} C = 0.25 F \\ L = 2 H \end{matrix}$$


$$\begin{cases} i_1(1+2\omega j) - i_2 = 12 \\ -i_1 + i_2(3-\frac{4}{\omega}j) = 0 \end{cases} \rightarrow i_2 = \frac{\begin{vmatrix} 1+2\omega j & 12 \\ -1 & 0 \end{vmatrix}}{\begin{vmatrix} 1+2\omega j & -1 \\ -1 & 3-\frac{4}{\omega}j \end{vmatrix}} = \frac{12}{10 + (6\omega - \frac{4}{\omega})j} A$$

$$i_2 = i_0$$

$$V_0(\omega) = \left(-\frac{4}{\omega}j\right) \left(\frac{12}{10 + (6\omega - \frac{4}{\omega})j}\right) = \frac{-48j}{10\omega + (6\omega^2 - 4)j} = \frac{48}{4 - 6\omega^2 + 10\omega j}$$

$$V_0 = \frac{\sqrt{48}}{\sqrt{(4-6\omega^2)^2 + 100\omega^2}} \angle -\arctan \frac{10\omega}{4-6\omega^2}$$

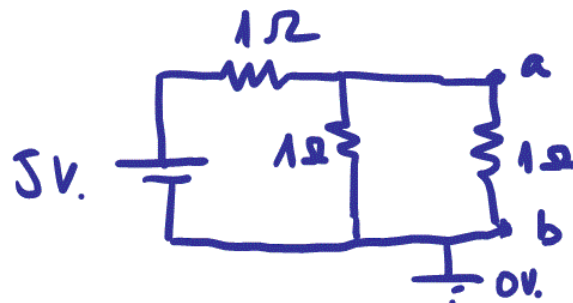2. (5 points) Given the following circuit. Find (across nodes a and b): (a) the Thevenin equivalent, (b) the Norton equivalent.



(a)  $R_{TH}$

$$\frac{1}{R_{TH}} = \frac{1}{1\Omega} + \frac{1}{1\Omega} + \frac{1}{1\Omega}$$

$$R_{TH} = \frac{1}{3} \Omega$$

$V_{TH}$

$$V_{TH} = V_{ab}$$

$$V_{ab} = 5V \cdot \frac{1/2 \Omega}{3/2 \Omega} = \frac{5}{3} V = V_{TH}$$

Thevenin equivalent:



(b)  $R_{TH} = R_N = \frac{1}{3} \Omega$



$$\frac{3}{2} \Omega \cdot i_N - \frac{1}{2} \Omega \cdot I_N = 5V$$

$$(I_N - i_N) \cdot \frac{1}{2} = 0 \rightarrow I_N = i_N$$

$$\frac{3}{2} \Omega \cdot I_N - \frac{1}{2} \Omega \cdot I_N = 5V \rightarrow I_N = 5A$$

Norton equivalent:

