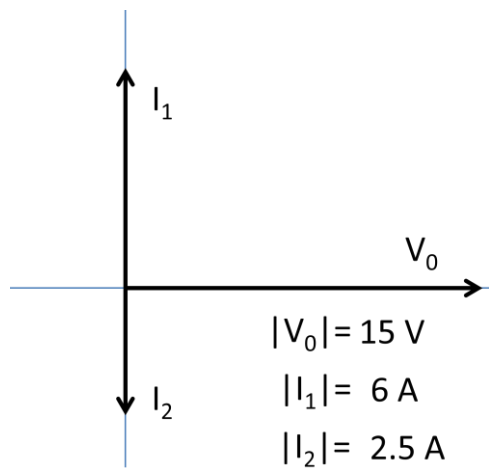


Theoretical Question 1: (1 point)

Given the following phasor diagram corresponding to an AC circuit with two parallel branches:


- Draw its corresponding circuit diagram, show the current in every branch. (0.25 points)
- Calculate the magnitude of the total current in the circuit and draw the associated phasor diagram (Use as reference V_0). (0.25 points)
- Draw the time-dependent graphs for V_0 , I_1 , I_2 and Total current (I_{TOT}). (0.5 Points)

NOTE: The values given for current and voltage are maximum values.




Solution:

a)

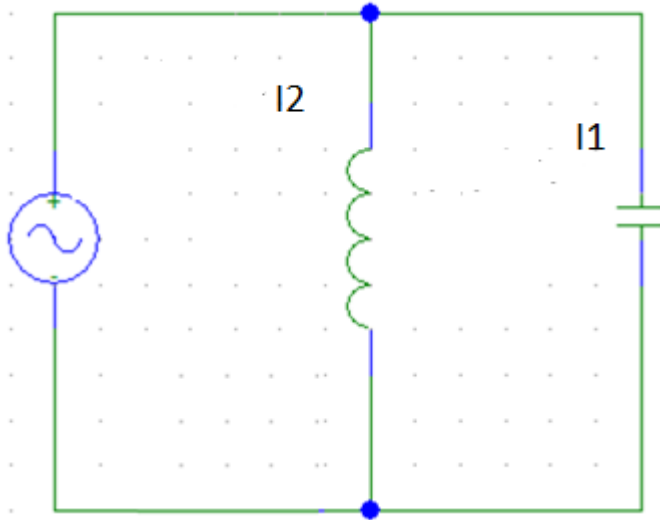


b)
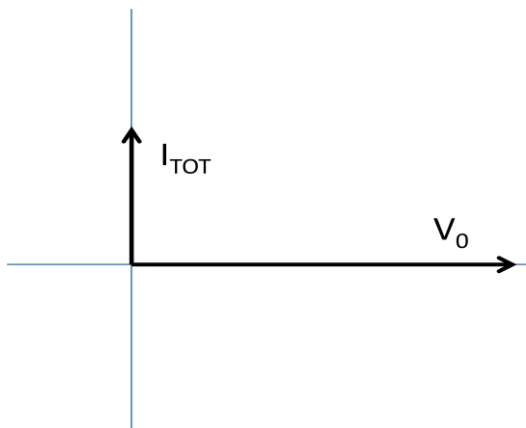
$$I_{TOT} = \vec{I}_1 + \vec{I}_2 = 6A \angle 90^\circ + 2.5A \angle -90^\circ = 3.5A \angle 90^\circ$$




c)

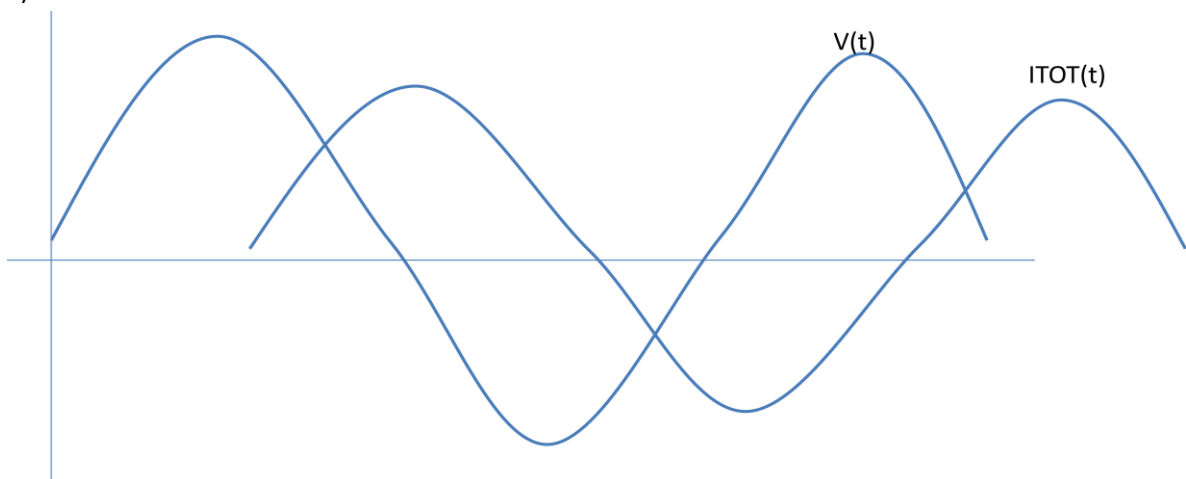

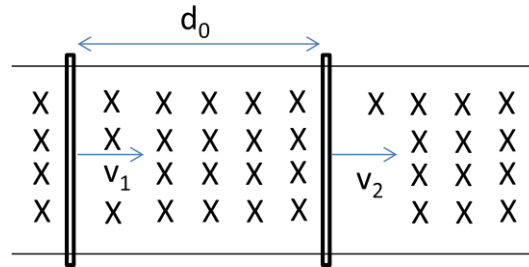Problem 1 (3 points):

Two parallel wires of negligible resistance are connected with two rods of length 10 cm and are moving with speeds $v_1 = 0.1 \text{ m/s}$ and $v_2 = 0.2 \text{ m/s}$. In the loop there is a uniform and homogeneous magnetic field $B = 10 \text{ mT}$ as shown in the figure, calculate:



- The magnetic flux through the loop defined by the rods and cables over time if they are initially separated by a distance $d_0 = 10 \text{ cm}$. (1 point)
- The induced electromotive force over time. (1 Point)
- If the resistivity of the rods is $\rho = 1.7 \cdot 10^{-8} \Omega \text{m}$ y its section $S = 10^{-6} \text{ m}^2$, calculate the current in the loop over time. (1 Point)



Solution:

a)

$$\phi = BS = Bl(d_0 + vt) = 10 \cdot 10^{-3} \times 0.1 \times (0.1 + 0.1t) = 10^{-4} + 10^{-4}t \text{ Wb}$$

b)

$$\varepsilon = -\frac{d}{dt}\phi = -\frac{d}{dt}(10^{-4} + 10^{-4}t) = -10^{-4}V$$

c)

$$R = \rho \frac{L}{S} = 1.7 \cdot 10^{-8} \frac{0.1}{10^{-6}} = 1.7 \cdot 10^{-3} \Omega$$

$$R_{TOT} = R \times 2 = 3.4 \cdot 10^{-3} \Omega.$$


$$\varepsilon = IR_{TOT} \Rightarrow I = \frac{|\varepsilon|}{R_{TOT}} = \frac{10^{-4}}{3.4 \cdot 10^{-3}} = 0.0294A = 29.4mA, \text{ counterclockwise}$$

Problem 2: (3 points)

Given the circuit of figure where the following events and conditions occurs:

$t \leq 0$	The 2 nF capacitor is uncharged, Switch S1 is open, Switch S2 is closed.
$t = 0$	Switch S1 is closed, S2 continued closed.
$t = 1000$ ns	Switch S2 opens, S1 continued closed.
$t = 10000$ ns	Switch S2 is closed, S1 continued closed.

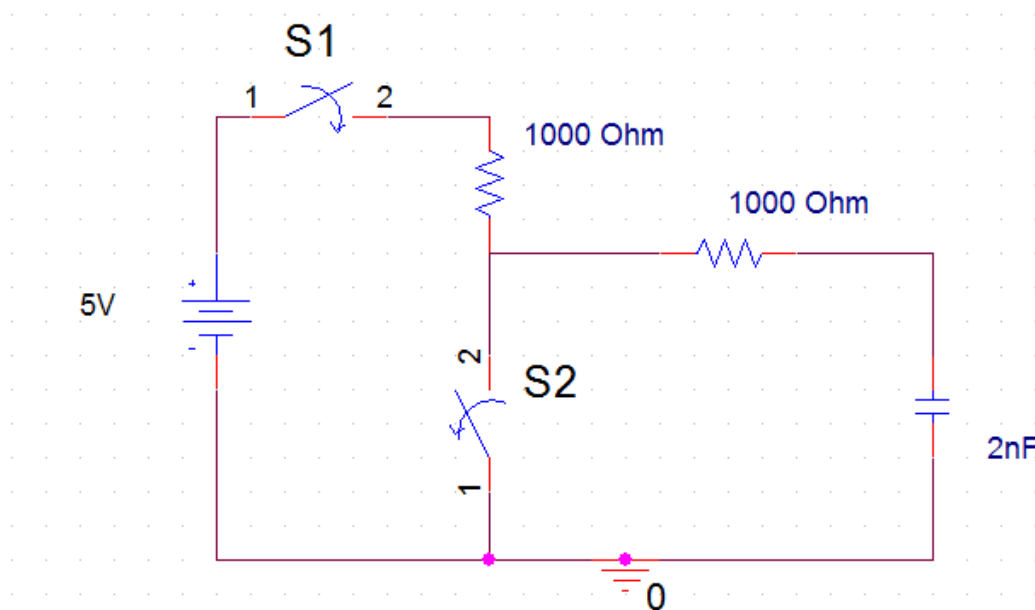- Study the behavior of the voltage (equations for $V_C(t)$) across the terminals of the 2 nF capacitor along time interval $[t_i = 0 \text{ ns}, t_f = 24000 \text{ ns}]$. (2 points)
- Find the numeric value of this voltage at $t = 0 \text{ ns}$, $t = 1000 \text{ ns}$, $t = 10000 \text{ ns}$, and $t = 24000 \text{ ns}$ (1 Point)





Solution:

(a)

$t \leq 0$	$V_C(t) = 0 \text{ V.}$
$t = 0 - 1000 \text{ nsec}$	$V_C(t) = 0 \text{ V.}$
$t = 1000_+ \text{ nsec} - 10000 \text{ nsec}$	$Z_1 = (1000 + 1000) \cdot 2 \cdot 10^{-9} \text{ s}$ $V_C(t) = 5 \left(1 - e^{-\frac{1}{Z_1}(t - 1000 \cdot 10^{-9})} \right) \text{ V.}$
$t = 10000_+ \text{ nsec} - 24000 \text{ nsec}$	$Z_2 = 1000 \cdot 2 \cdot 10^{-9} \text{ s}$ $V_C(t) = 4.47 \cdot e^{-\frac{1}{Z_2}(t - 10000 \cdot 10^{-9})} \text{ V.}$

(b)

$t = 0 \text{ nsec}, V_C = 0 \text{ V.}$

$t = 1000 \text{ nsec}, V_C = 0 \text{ V.}$


$t = 10000 \text{ nsec}, V_C = 4.47 \text{ V.}$

$t = 24000 \text{ nsec}, V_C = 0.0046 \text{ V.}$


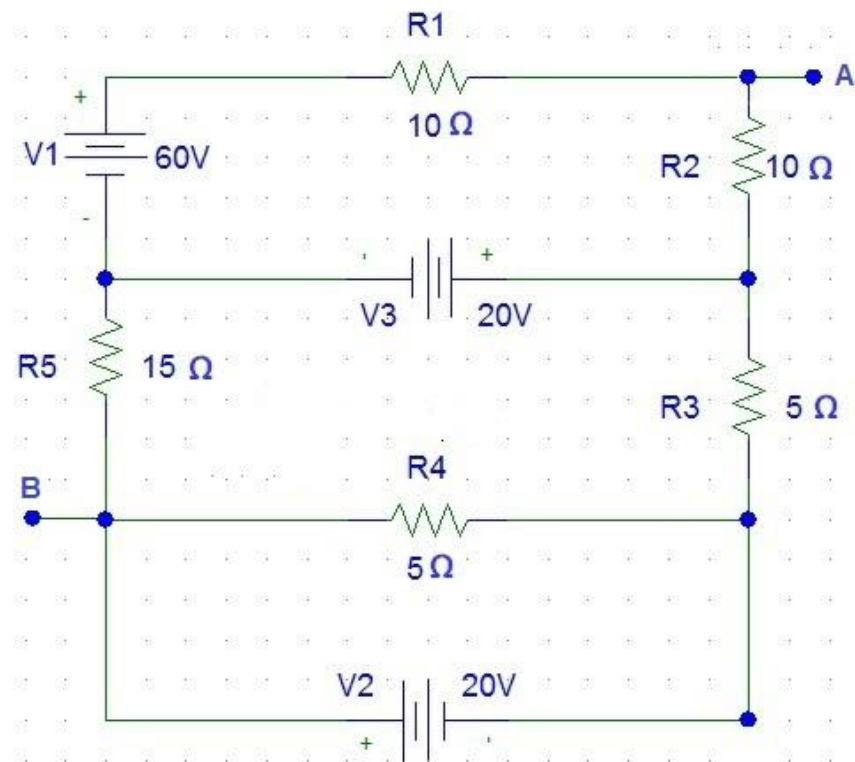
Problem 3: (3 points)

Given the circuit of the figure:

- Calculate the Thevenin's equivalent of this circuit across terminals A and B (1.5 points)
- Calculate also the current through the resistor R4. (1.5 points)



Solution:

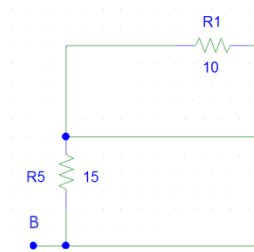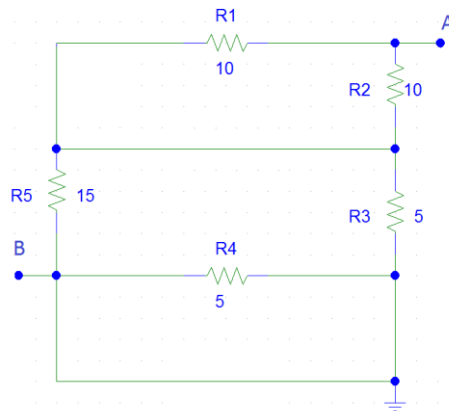


$$\frac{1}{R_{12}} = \frac{1}{10} + \frac{1}{10} = \frac{1}{5}$$


$$R_{12} = 5 \Omega$$

$$\frac{1}{R_{35}} = \frac{1}{5} + \frac{1}{15} = \frac{4}{15}$$

$$R_{35} = 3,75 \Omega$$

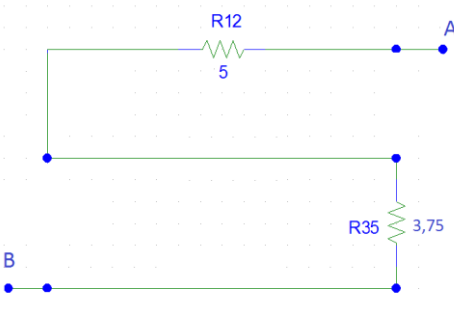
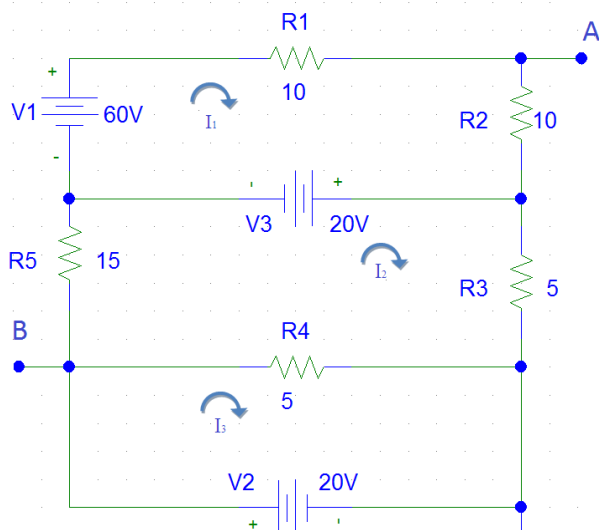
$$R_{Th} = R_{12} + R_{35} = 5 + 3,75 = 8,75 \Omega$$



$$20 I_1 = 40, I_1 = 2 A$$

$$\left. \begin{array}{l} 25 I_2 - 5 I_3 = 20 \\ 5(I_3 - I_2) = 20 \end{array} \right\}$$

$$I_2 = 2 A$$

$$I_3 = 6 A$$

$$V(R5) = R5 \cdot I_2 = 15 \cdot 2 = 30 \text{ V}$$

$$V(R1) = R1 \cdot I_1 = 10 \cdot 2 = 20 \text{ V}$$

$$V_{Th} = V1 - V(R1) - V(R5) = 60 - 20 - 30 = 10 \text{ V}$$

$$I_{R4} = I_3 - I_2 = 2 \text{ A}$$

