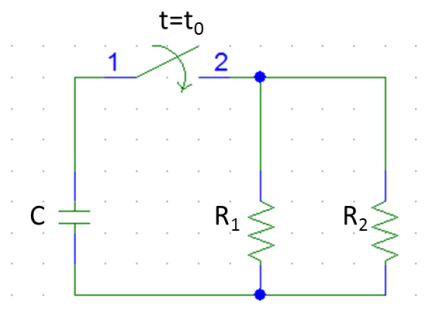


### Question 1: (1 point)

Given a capacitor  $C$  charged with an initial charge  $Q_0$  connected to two resistors  $R_1$  and  $R_2$  as shown in Fig. At time  $t = t_0$  s the switch is closed so that the capacitor is discharged through the resistors.



Calculate the next variables, as a function of the parameters  $Q_0$ ,  $C$ ,  $R_1$ ,  $R_2$  and  $t_0$ :

- The voltage across the capacitor as a function of time.
- Maximun current.
- The current through each resistor as a function of time.

Solution:

$$a) \quad V(t) = \frac{Q_0}{C} e^{-\frac{t-t_0}{R_1 R_2 C} (R_1 + R_2)}$$

$$b) \quad I_{MAX} = \frac{Q_0}{\tau} = \frac{Q_0 (R_1 + R_2)}{R_1 R_2 C}$$

c)


$$I_1(t) = \frac{V(t)}{R_1} = \frac{Q_0}{R_1 C} e^{-\frac{t-t_0}{R_1 R_2 C} (R_1 + R_2)}$$

$$I_2(t) = \frac{V(t)}{R_2} = \frac{Q_0}{R_2 C} e^{-\frac{t-t_0}{R_1 R_2 C} (R_1 + R_2)}$$

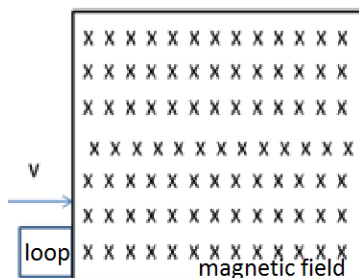
### Problem 1 (3 points):

Given a finite magnetic field of 0,6T in a rectangular space of dimensions 20 m x 10 m, direction perpendicular to the paper, and a square loop of 10 cm side and resistance 10  $\Omega$ . Given the next cases:

- Case 1: The loop moves horizontally to the right along +X axis in the magnetic field from the initial position of the next figure with a constant speed of 2 m/s.



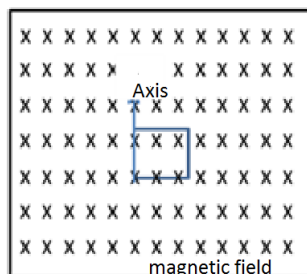- Case 2: The loop moves vertically along +Y direction from the initial position of the previous figure with a constant speed of 1 m/s.
- Case 3: The loop is introduced into the magnetic field and rotates inside around its vertical left axis with an angular velocity of 2 rad/s, as shown in next figure.



Calculate:

- The induced emf in the loop for each case (2 points)
- The magnitude and direction of the induced current in the loop (1 point)

Solution:

a)

- Case 1

- $t=0, t=0,1/2 \text{ s}$

$$\varepsilon = -B * l * v = -0,6 * 0,1 * 20 = -0,12 \text{ V}$$

- $t=0,05 \text{ s}, t=(20-0,2)/2=9,9 \text{ s} \rightarrow \varepsilon=0 \text{ V}$
- $t=9,9 \text{ s} \rightarrow t=9,9+0,05$

$$\varepsilon = B * l * v = 0,6 * 0,1 * 20 = 0,12 \text{ V}$$

- $t=9,95 \rightarrow \infty \varepsilon=0 \text{ V}$
- Case 2  $\varepsilon=0 \text{ V}$
- Case 3  $t=4,95 \text{ s} \rightarrow \infty \varepsilon = \omega B S \text{ Sen}(\omega t) = 2 * 0,6 * 0,01 \text{ sen } 2t = 0,012 \sin(2t) \text{ V}$

b)

X:

$t=0 \rightarrow 0,05 \text{ s} ; I=-0,012 \text{ A}$  counterclockwise

$t=0,05 \rightarrow 9,9 \text{ s} ; I=0 \text{ A}$



$t=9,9 \text{ s} \rightarrow 9,95 \text{ I}=0,012 \text{ A}$  clockwise  
 $t=9,95 \rightarrow \infty \text{ I}=0$

Y:

$t=0 \rightarrow \infty \text{ I}=0$


Rotating:  $I = 0,0012 \sin(2t) \text{ A}$ , alternating

## Problem 2: (3 points)

Given the circuit in next figure where the voltage source supplies  $v(t)=8 \sin(t+\pi/4) \text{ V}$ .

Calculate:

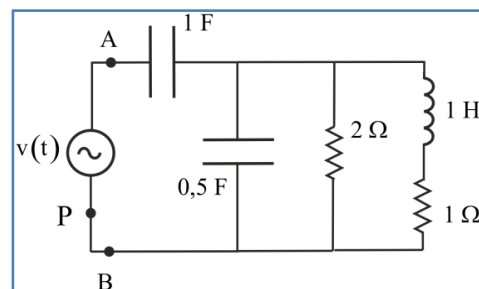- The equivalent impedance across nodes A and B. (1 point)
- The current in the circuit (0.75 points).
- The average power (0.75 points)
- What element has to be connected across nodes P and B replacing the previous short-circuit so that the voltage source supply the maximum current? (0.5 points)



Solution:

a)

$$\vec{Z}_T = \vec{Z}_C + 1/\vec{Y}_P = 1 - j = \sqrt{2} \angle -45^\circ \Omega$$

b)

$$I_T = V/Z_T = (8 \angle -45^\circ) / \sqrt{2} \angle -45^\circ = 4\sqrt{2} \angle 0^\circ \text{ A}$$

c)

$$P_a = \left(\frac{1}{2}\right) I_0 V_0 \cos \varphi = I_0^2 R = \left(\frac{1}{2}\right) 4 \cdot \sqrt{2} \cdot 8 \cdot \frac{\sqrt{2}}{2} = \left(\frac{1}{2}\right) (4 \cdot \sqrt{2})^2 \cdot 1 = 16 \text{ W}$$

$$\cos \varphi = \cos 45^\circ = \sqrt{2}/2$$


d)

$$\text{Im}[\bar{Z}_T] = 0 \quad L=1\text{H or } Z=1+j$$

### Problem 3: ( 3 points).

Given the circuit in next figure.

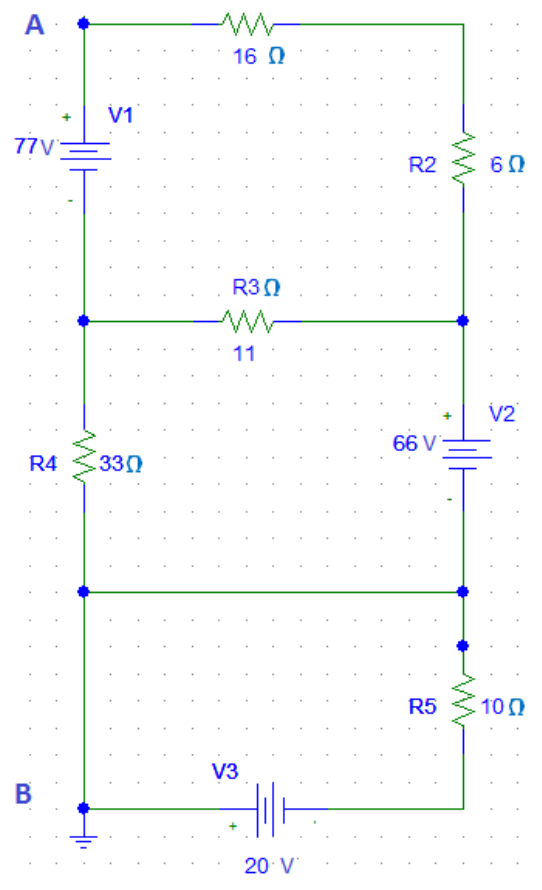
1. Calculate and draw the Thévenin equivalent across nodes A and B (2p)
2. Calculate the current through R2 and R5 (0,5 p)
3. Calculate and draw the Norton equivalent (0,5 p)



Solution:

$$1. \quad V_{AB} = V_1 + R_4 \cdot I_2 = 77 + 33 \cdot 1 = 110 \text{ V}$$

$$R_{AB} = 6 \Omega$$

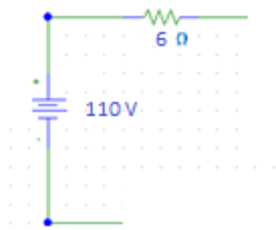

2.

$$I_{R2} = I_1 = 2 \text{ A}$$

$$I_{R5} = I_3 = 2 \text{ A}$$

3.

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{110}{6} = 18,3 \text{ A}, R_N = 6 \text{ ohm}$$

